

Electrical Engineering 141, Homework 1

Michael Wu
UID: 404751542

January 25th, 2019

Problem 1

a) First we have the following.

$$\begin{aligned} Y_1 &= G_2 G_1 (R_1 - H_1 Y_1) \\ &= \frac{G_1 G_2}{1 + G_1 G_2 H_1} R_1 \end{aligned}$$

Then we can write the transfer function for Y_2 as follows.

$$\begin{aligned} Y_2 &= G_4 (G_3 (G_6 Y_1 - H_2 Y_2) + G_5 G_1 (R_1 - H_1 Y_1)) \\ (1 + G_4 G_3 H_2) Y_2 &= G_4 G_3 G_6 Y_1 + G_4 G_5 G_1 R_1 - G_4 G_5 G_1 H_1 Y_1 \\ (1 + G_4 G_3 H_2) Y_2 &= (G_4 G_3 G_6 - G_4 G_5 G_1 H_1) Y_1 + G_4 G_5 G_1 R_1 \\ \frac{Y_2}{R_1} &= \left(\frac{G_4 G_3 G_6 - G_4 G_5 G_1 H_1}{1 + G_4 G_3 H_2} \right) \frac{Y_1}{R_1} + \frac{G_4 G_5 G_1}{1 + G_4 G_3 H_2} \end{aligned}$$

Then we can plug in our earlier expression to obtain the following.

$$\begin{aligned} \frac{Y_2}{R_1} &= \left(\frac{G_4 G_3 G_6 - G_4 G_5 G_1 H_1}{1 + G_4 G_3 H_2} \right) \frac{G_1 G_2}{1 + G_1 G_2 H_1} + \frac{G_4 G_5 G_1}{1 + G_4 G_3 H_2} \\ &= \frac{G_1 G_2 G_4 G_3 G_6 - G_2 G_4 G_5 G_1^2 H_1 + G_4 G_5 G_1 + G_2 G_4 G_5 G_1^2 H_1}{(1 + G_4 G_3 H_2)(1 + G_1 G_2 H_1)} \\ &= \frac{G_1 G_2 G_3 G_4 G_6 + G_1 G_4 G_5}{(1 + G_3 G_4 H_2)(1 + G_1 G_2 H_1)} \end{aligned}$$

b) If we let

$$G_5(s) = -G_2G_3G_6$$

then the previous transfer function will be zero.

Problem 2

a) Across the first resistor we have

$$V_i - V_a = I_a Z_1$$

due to Ohm's law. Across the second resistor we also have

$$V_o - V_a = I_b Z_2$$

due to Ohm's law. Since the impedance of the OpAmp is infinity, we know that the current into the negative side is zero. Then Kirchhoff's law gives us

$$I_a + I_b = 0$$

which we can rewrite using the previous equations to obtain the following.

$$\begin{aligned} \frac{V_i - V_a}{Z_1} + \frac{V_o - V_a}{Z_2} &= 0 \\ (V_i - V_a) * Z_2 + (V_o - V_a) * Z_1 &= 0 \\ Z_2 V_i + Z_1 V_o &= (Z_1 + Z_2) V_a \\ V_a &= \frac{Z_2}{Z_1 + Z_2} V_i + \frac{Z_1}{Z_1 + Z_2} V_o \end{aligned}$$

b)

$$\begin{aligned} V_o &= -a \left(\frac{Z_2}{Z_1 + Z_2} V_i + \frac{Z_1}{Z_1 + Z_2} V_o \right) \\ \left(1 + \frac{a Z_1}{Z_1 + Z_2} \right) V_o &= \frac{-a Z_1}{Z_1 + Z_2} V_i \\ \frac{V_o}{V_i} &= \frac{\frac{-a Z_1}{Z_1 + Z_2}}{1 + \frac{a Z_1}{Z_1 + Z_2}} \end{aligned}$$

c) This is equivalent to assuming that $V_a = 0$ in our previous calculations. Then we have across the first resistor

$$V_i = I_a Z_1$$

due to Ohm's law. Across the second resistor we also have

$$V_o = I_b Z_2$$

due to Ohm's law. Then Kirchhoff's law gives us

$$I_a + I_b = 0$$

which we can rewrite as follows.

$$\begin{aligned}\frac{V_i}{Z_1} + \frac{V_o}{Z_2} &= 0 \\ \frac{V_o}{Z_2} &= -\frac{V_i}{Z_1} \\ \frac{V_o}{V_i} &= -\frac{Z_2}{Z_1}\end{aligned}$$

d) Let I_1 be a current flowing down across Z_1 . Let I_2 be a current flowing to the left across Z_2 . Then we have that

$$V_o - V_a = I_2 Z_2$$

and that

$$V_a = I_1 Z_1$$

and from Kirchhoff's law we have that

$$I_2 = I_1$$

This means that we know that

$$\begin{aligned}\frac{V_o - V_a}{Z_2} &= \frac{V_a}{Z_1} \\ \frac{V_o}{Z_2} &= \frac{V_a}{Z_1} + \frac{V_a}{Z_2} \\ V_a &= \frac{Z_1}{Z_1 + Z_2} V_o\end{aligned}$$

Additionally across the OpAmp we know that

$$\begin{aligned}
 V_o &= a(V_i - V_a) \\
 V_o &= a \left(V_i - \frac{Z_1}{Z_1 + Z_2} V_o \right) \\
 \left(1 + \frac{aZ_1}{Z_1 + Z_2} \right) V_o &= aV_i \\
 \frac{V_o}{V_i} &= \frac{a}{1 + \frac{aZ_1}{Z_1 + Z_2}} \\
 \frac{V_o}{V_i} &= \frac{a(Z_1 + Z_2)}{(1 + a)Z_1 + Z_2}
 \end{aligned}$$

As the gain a becomes very large the limit of this becomes

$$\frac{V_o}{V_i} = \frac{Z_1 + Z_2}{Z_1}$$

e) This is the same as the inverting amplifier that we studied earlier, except with impedances

$$Z_1 = \frac{\frac{R_1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}}$$

and

$$Z_2 = R_2 + \frac{1}{j\omega C_2}$$

which can be rewritten in terms of s to be

$$\begin{aligned}
 Z_1 &= \frac{\frac{R_1}{sC_1}}{R_1 + \frac{1}{sC_1}} = \frac{R_1}{1 + sR_1C_1} \\
 Z_2 &= R_2 + \frac{1}{sC_2} = \frac{1 + sR_2C_2}{sC_2}
 \end{aligned}$$

Then our transfer function is given by the following

$$\begin{aligned}
 \frac{V_o(s)}{V_i(s)} &= - \frac{(1 + sR_2C_2)(1 + sR_1C_1)}{sR_1C_2} \\
 &= - \frac{1 + s(R_1C_1 + R_2C_2) + s^2R_1C_1R_2C_2}{sR_1C_2} \\
 &= - \left(\frac{C_1}{C_2} + \frac{R_1}{R_2} \right) - R_2C_1s - \frac{1}{sR_1C_2}
 \end{aligned}$$

Therefore this is equivalent to

$$\begin{aligned}\frac{V_0(s)}{V_i(s)} &= K_P + K_D s + \frac{K_I}{s} \\ K_P &= -\frac{C_1}{C_2} - \frac{R_1}{R_2} \\ K_D &= -R_2 C_1 \\ K_I &= -\frac{1}{R_1 C_2}\end{aligned}$$

f) We have that

$$v_o = -\frac{R_b}{R_a} v_2$$

since there is an inverting amplifier in the middle of the circuit. Furthermore we have that $v_2 = \frac{Q_1}{C_1}$, and so

$$v'_2 = \frac{I_1}{C_1}$$

where I_1 is the current going through the capacitor C_1 . The current going through the resistor R_1 is equal to $I_1 + I_a$, where I_a is the current going through R_a . We can solve

$$\begin{aligned}v_2 - v_o &= I_a(R_a + R_b) \\ \left(1 + \frac{R_b}{R_a}\right) v_2 &= I_a(R_a + R_b) \\ I_a &= \frac{v_2}{R_a}\end{aligned}$$

to obtain the expression

$$v_1 - v_2 = \left(C_1 v'_2 + \frac{v_2}{R_a}\right) R_1$$

from the left side of the circuit. Similarly the right side of the circuit gives us

$$-\frac{R_b}{R_a} v_2 - v_3 = C_2 v'_3 R_2$$

Solving for v'_2 and v'_3 yields the system of equations shown below.

$$\begin{aligned} v'_2 &= \left(-\frac{1}{R_1 C_1} - \frac{1}{R_a C_1} \right) v_2 + \frac{1}{R_1 C_1} v_1 \\ v'_3 &= -\frac{R_b}{R_a R_2 C_2} v_2 - \frac{1}{R_2 C_2} v_3 \end{aligned}$$

which is equivalent to the State-Space form

$$\frac{dx}{dt} = \begin{bmatrix} -\frac{1}{R_1 C_1} - \frac{1}{R_a C_1} & 0 \\ -\frac{R_b}{R_a R_2 C_2} & -\frac{1}{R_2 C_2} \end{bmatrix} x + \begin{bmatrix} \frac{1}{R_1 C_1} \\ 0 \end{bmatrix} v_1$$

Problem 3

a)

b)

c)

d)

e)

Problem 4

We can convert each equation into a linear approximation by taking the appropriate derivatives evaluated at our initial point. For the first equation we have

$$x'_1 \approx u \frac{\partial f_1}{\partial u} + x_2 \frac{\partial f_1}{\partial x_2} = 0 + x_2$$

For the second equation we have

$$x'_2 \approx u \frac{\partial f_2}{\partial u} + x_4 \frac{\partial f_2}{\partial x_4} = -\pi u - \pi x_4$$

For the third equation we have

$$x'_3 \approx u \frac{\partial f_3}{\partial u} + x_2 \frac{\partial f_3}{\partial x_2} = \pi u + \pi x_2$$

For the fourth equation we have

$$x'_4 \approx x_1 \frac{\partial f_4}{\partial x_1} + x_3 \frac{\partial f_4}{\partial x_3} = 2x_1 + 4x_3$$

This yields the linear system

$$\delta x' = \begin{bmatrix} 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & -\pi \\ 0 & \pi & 0 & 0 \\ 2 & 0 & 4 & 0 \end{bmatrix} \delta x + \begin{bmatrix} 0 \\ -\pi \\ \pi \\ 0 \end{bmatrix} \delta u$$

Problem 5

Problem 6

a)

b)

Problem 7

a)

b)

c)